

4-bit Carry Look Ahead Adder Design

VLSI Design Course Project

Aanchal Amit Mundhada

2023112016

Electronics and Communication Dual Degree

International Institute of Information Technology, Hyderabad

aanchal.mundhada@research.iiit.ac.in

Abstract — This report presents a design of 4-bit carry look ahead adder which has inputs taken from D flip flop and outputs also pass through the D flip flop.

Keywords—adder, carry look ahead adder, D flip flop, sum block, CLA, Propagate Generate

I. INTRODUCTION

The adder in this project is designed using basic digital logic components like AND gates, OR gates, and inverters, which are combined to form full adders. Each full adder calculates the sum and carry for a pair of input bits. The adder follows a ripple-carry structure, where the carry output from one bit is passed to the next, starting from the least significant bit to the most significant bit. If the numbers to be added are $a_3a_2a_1a_0$ and $b_3b_2b_1b_0$, then the propagate (pi) and generate (gi) signals for each bit position can be defined as,

$$pi = ai \oplus bi$$

$$gi = ai . bi$$

and the carry out ($c(i+1)$) of the i^{th} bit position can be written as,

$$c(i+1) = (pi . ci) + gi, i = 0, 1, 2, 3$$

Thus, $c(i+1)$ can be expressed entirely in terms of the pi and gi functions and sum can be represented as follows,

$$sum_i = pi \oplus ci$$

TSPC D flip-flops are included to manage timing and hold intermediate values, ensuring the circuit operates reliably in clocked systems. This modular design allows for easy expansion to handle larger bit-widths, making it adaptable for various applications.

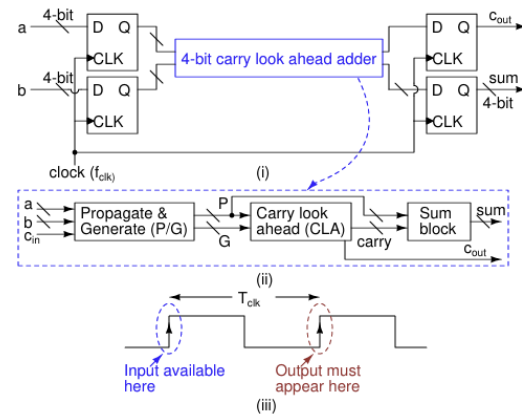


Fig. 1. Adder

II. DESIGN DETAILS

The circuit is made by combining logic gates AND, OR and XOR. It also uses inverters and D flip flops.

The propagate generate block takes input a_i and b_i from D flip flop and using 2 input AND gate we calculate g_i as $g_i = a_i \cdot b_i$. On using 2 input XOR gate we calculate p_i as $p_i = a_i \oplus b_i$.

For carry look ahead block the inputs are p_i , g_i and c_0 . We calculate c_1 , c_2 , c_3 and c_4 .

$c_1 = g_0 + p_0c_0$, here we use 2 input AND gate for p_0c_0 and then 2 input OR gate to combine g_0 and p_0c_0 to calculate our c_1 .

$c_2 = g_1 + p_1g_0 + p_1p_0c_0$, here we use 3 input AND gate for $p_1p_0c_0$ and 2 input AND gate for p_1g_0 , then 3 input OR gate to combine g_1 , p_1g_0 and $p_1p_0c_0$ to calculate our c_2 .

$c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$, here we use 4 input AND gate for $p_2p_1p_0c_0$, 3 input AND gate for $p_2p_1g_0$ and 2 input AND gate for p_2g_1 , then 4 input OR gate to combine g_2 , p_2g_1 , $p_2p_1g_0$ and $p_2p_1p_0c_0$ to calculate our c_3 .

$c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$, here we use 5 input AND gate for $p_3p_2p_1p_0c_0$, 4 input AND gate for $p_3p_2p_1g_0$, 3 input AND gate for $p_3p_2g_1$ and 2 input AND gate for p_3g_2 , then 5 input OR gate to combine g_3 , p_3g_2 , $p_3p_2g_1$, $p_3p_2p_1g_0$ and $p_3p_2p_1p_0c_0$ to calculate our c_4 .

(Note: It is given that c_0 is zero, so we don't really need 5 input AND and OR gates. I have used % input gates in NGSpice but not in MAGIC)

For sum block, we use 2 input XOR gate with inputs c_i and p_i calculated from previous blocks as $sum_i = p_i \oplus c_i$.


We get outputs s_0 , s_1 , s_2 , s_3 and c_4 which is passed through D flip flop.

A. Gates


For all the gates we use CMOS Topology. Their circuit diagram along with sizing are given below.

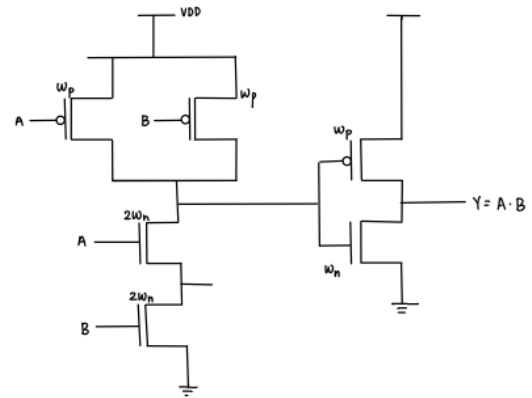i. AND gates


Sizing: W_p and NW_n , N is number of inputs.



2 - Input AND Gate
(a)

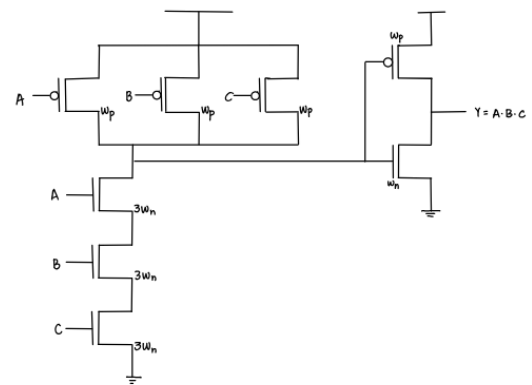

3- Input AND Gate
(b)

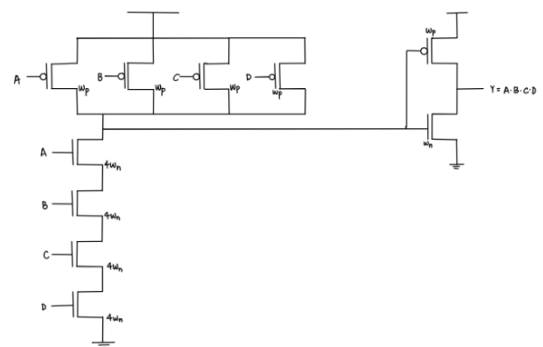


4- input AND Gate
(c)

Fig. 2. (a) 2 input AND (b) 3 input AND (c) 4 input AND

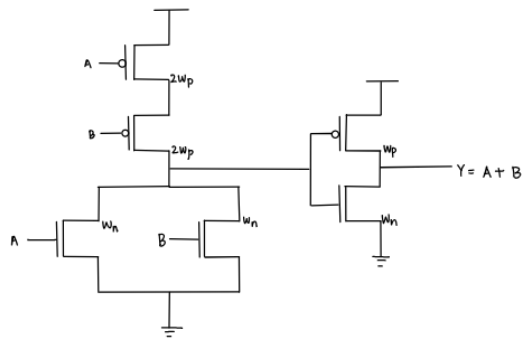
ii. OR gates

Sizing: NW_p and W_n , N is number of inputs.




2-Input OR Gate

(a)

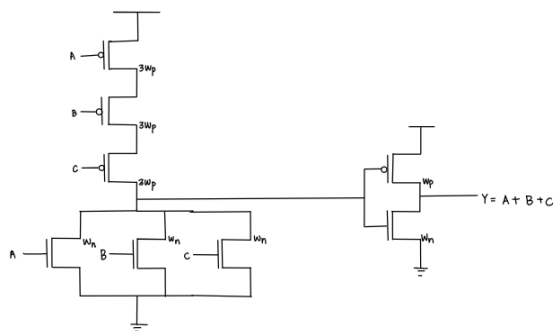

3-Input OR Gate

(b)

 


4-Input OR Gate

(c)

Fig. 3. (a) 2 input OR (b) 3 input OR (c) 4 input OR

 iii. XOR gate


XOR gate made by using 2 inverters, 2 AND gates and 1 OR gate as shown in Fig. 4



XOR Gate

Fig. 4. 2 input XOR gate

B. TSPC flip flop

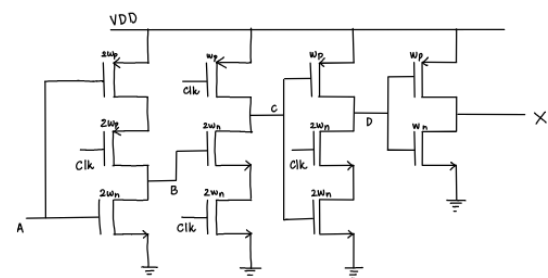

TSPC Flip Flop

Fig. 5. TSPC flip flop


III. PRE-LAYOUT SIMULATION IN NGSPICE

A. CLA adder

 
i. Propagate and generate

For, A=1110 and B=1011 we get following outputs,

$p_0=1, p_1=0, p_2=1, p_3=0$ and $g_0=0, g_1=1, g_2=0, g_3=1$



(a)

 

(b)

Fig. 6. (a) Propagate (b) Generate

ii. Carry look ahead

For, $p_0=0, p_1=1, p_2=1, p_3=1$ and $g_0=1, g_1=1, g_2=0, g_3=1, c_0=0$ we get the following outputs,

$c_1=1, c_2=1, c_3=1, c_4=1$

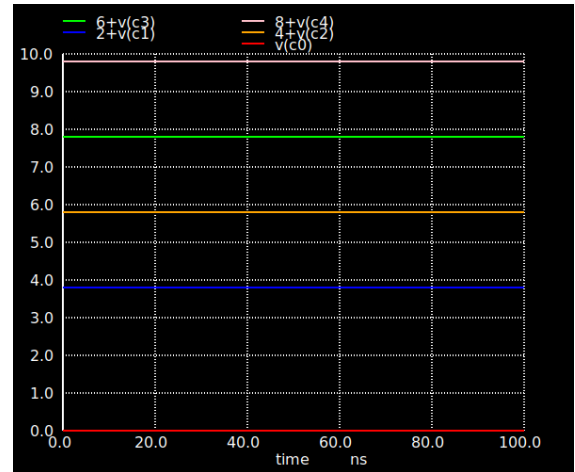


Fig. 7. Carry look ahead block

iii. Sum block

For $c_0=0, c_1=1, c_2=1, c_3=1$ and $p_0=1, p_1=1, p_2=0, p_3=1$ we get following outputs,

$s_0=1, s_1=0, s_2=1, s_3=0$

 


Fig. 8. Sum block

iv. Complete adder

For $A=1110$ and $B=1011$ we get $\text{sum}=1001$ and $\text{cout}=1$

 


Fig. 9. Adder (pre layout)

We get $tpd_{max}=0.72ns$ for $s3$.

tpd_rise	=	7.116351e-10	targ=	7.616351e-10	trig=	5.000000e-11
tpd_fall	=	7.343098e-10	targ=	1.088431e-08	trig=	1.015000e-08
tpd_max	=	7.22972e-10				

Fig. 10. tpd_{max} (pre layout)

B. D flip flop

As we can see, X is updated to A at positive edge only.

 


Fig. 11. D flip flop

IV. SETUP TIME, HOLD TIME AND PROPAGATION DELAY FROM CLK TO Q IN FLIPFLOP

We have used TSPC topology for our D-FlipFlop. Since there is no use of clk' , we have zero hold time ($thold = 0$).

For setup time, we did trial and error and found it to be $t_{setup} = 0.1019ns$. Any input given less than t_{setup} before next +ve edge, either input is not registered or output is being corrupted.

Propagation delay from clk to Q will be $0.087ns$.

tpd_rise	=	5.761607e-11	targ=	2.010762e-08	trig=	2.005000e-08
tpd_fall	=	1.167702e-10	targ=	4.016677e-08	trig=	4.005000e-08
total_prop_delay	=	8.71931e-11				

Fig. 12. Total propagation delay (pre layout)

V. STICK DIAGRAM OF ALL UNIQUE GATES AND FLIPFLOP

 


Fig. 13. Inverter stick diagram

 


Fig. 14. 2 input AND gate stick diagram

 


Fig. 15. 3 input AND gate stick diagram

 


Fig. 18. 3 input OR gate stick diagram

 


Fig. 16. 4 input AND gate stick diagram

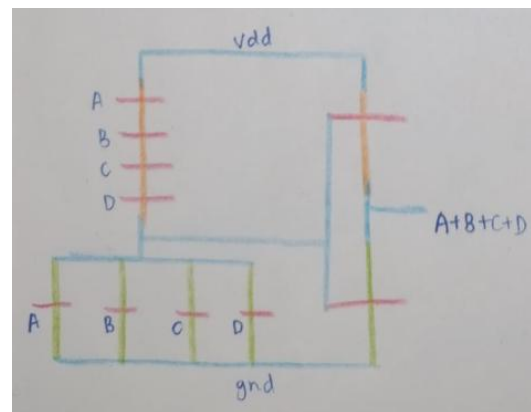


Fig. 19. 4 input OR gate stick diagram

 


Fig. 17. 2 input OR gate stick diagram

 


Fig. 20. TSPC flip flop stick diagram

VI. POST LAYOUT SIMULATION FOR MAGIC

A. CLA adder

i. Propagate and generate


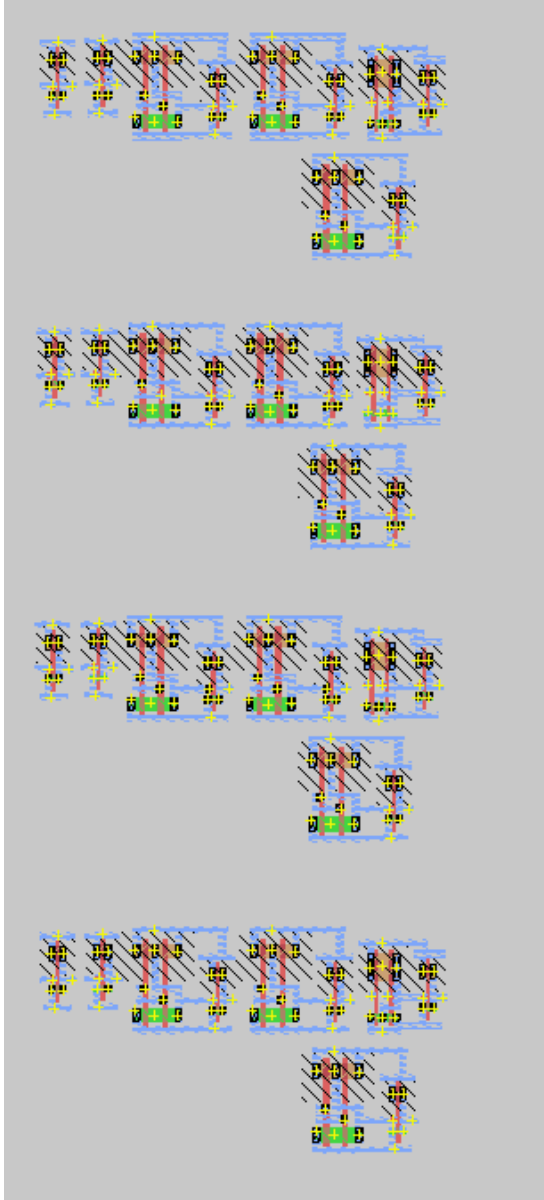



Fig. 21. Propagate Generate MAGIC layout

For, A=1110 and B=1011 we get following outputs,

 $p_0=1, p_1=0, p_2=1, p_3=0$ and $g_0=0, g_1=1, g_2=0, g_3=1$



(a)

 

(b)

Fig. 22. (a)Post layout propagate (b)Post layout generate

ii. Carry look ahead

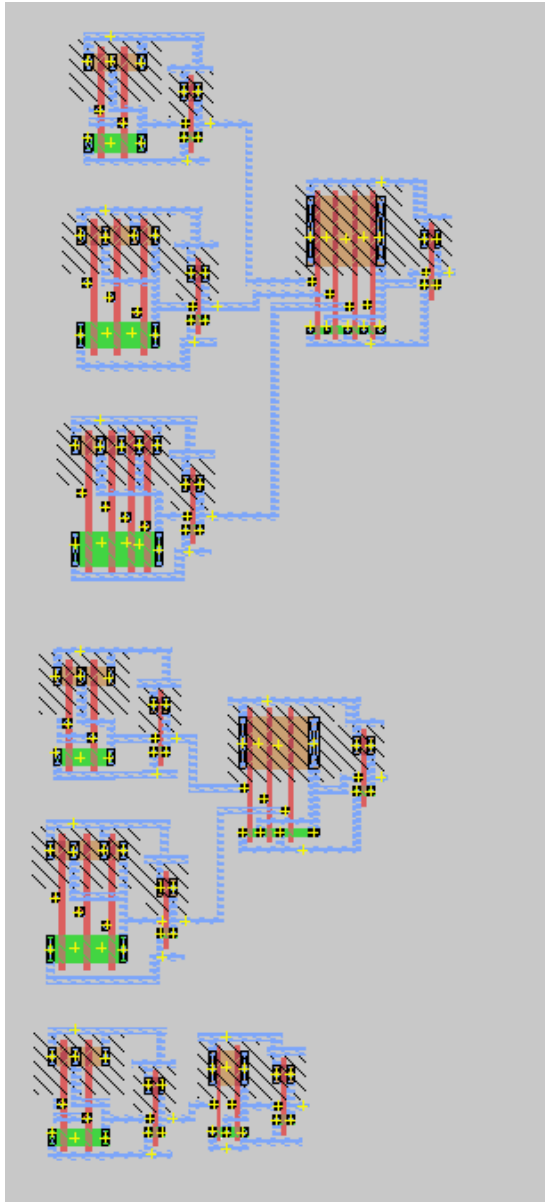


Fig. 23. Carry look ahead MAGIC layout

For, $p_0=0$, $p_1=1$, $p_2=1$, $p_3=1$ and $g_0=1$, $g_1=1$, $g_2=0$, $g_3=1$, $c_0=0$ we get the following outputs,

$c_1=1$, $c_2=1$, $c_3=1$, $c_4=1$

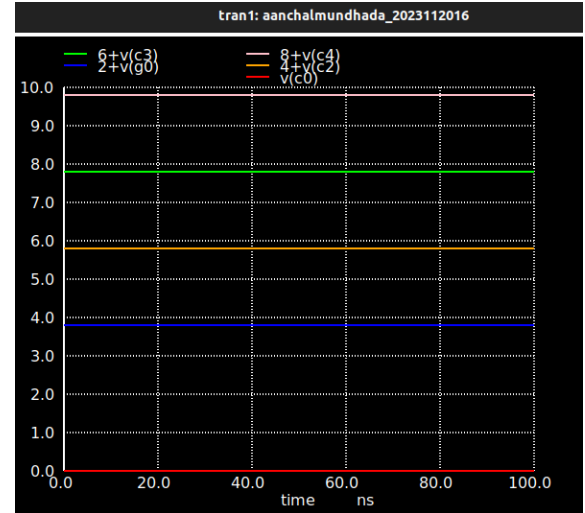


Fig. 24. Post layout carry look ahead block

iii. Sum block

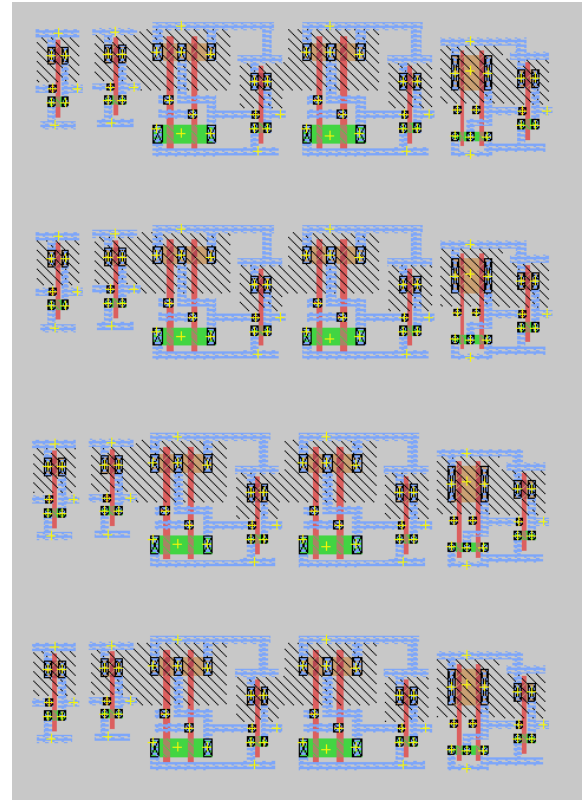


Fig. 25. Sum block MAGIC layout

For $c_0=0$, $c_1=1$, $c_2=1$, $c_3=1$ and $p_0=1$, $p_1=1$, $p_2=0$, $p_3=1$ we get following outputs,

$s_0=1$, $s_1=0$, $s_2=1$, $s_3=0$

 


Fig. 26. Post layout sum block

iv. Complete adder

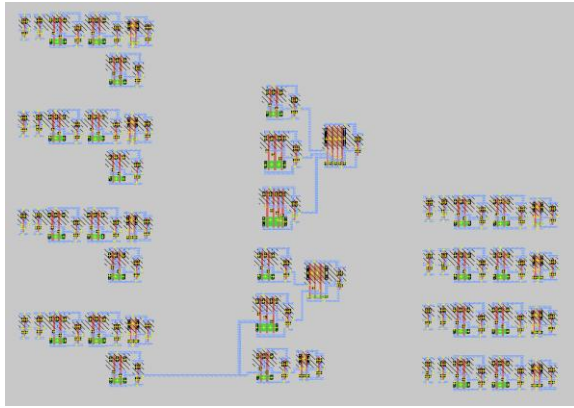


Fig. 27. Adder MAGIC layout

For A=1110 and B=1011 we get sum=1001 and cout=1

 


Fig. 28. Post layout adder

We get tpd_max=0.82ns for s3.

 


Fig. 29. tpd_max (post layout)

B. D flip flop

 


Fig. 30. D flip flop MAGIC layout

As we can see, X is updated to A at positive edge only.

 


Fig. 31. Post layout D flip flop

Total propagation delay will be 0.10ns.

 


Fig. 32. Total propagation delay (post layout)

	Pre-layout	Post-layout
Propagation delay for D flip flop	0.0872ns	0.1026ns
tpd_max for adder	0.723ns	0.8245ns

Table 1. Propagation delay and tpd_max comparison

VII. SIMULATIONS OF FINAL CIRCUIT IN NGSPICE

We combine the CLA-Adder with D-Flipflops to give input at positive edge and get output at second positive edge.

For A=1110 and B=1011 we get sum as 1001 and cout as 1 at the second positive edge of the clock. This means our circuit is working correctly.

 


Fig. 33. Final circuit (pre layout)

Worst case delay seen in pre-layout simulation is 0.723ns.

For maximum clock frequency we find minimum clock time.

$$tclk_min = thold + tpd_max + tpcq_max$$

$$tclk_min = 0 + 0.72ns + 0.087ns = 0.807ns$$

Hence, $fmax = 1239.16$ MHz.

Maximum clock frequency at which our circuit operates correctly is 1239.16 MHz.

VIII. FLOOR PLAN AND MAGIC LAYOUT FOR FINAL CIRCUIT

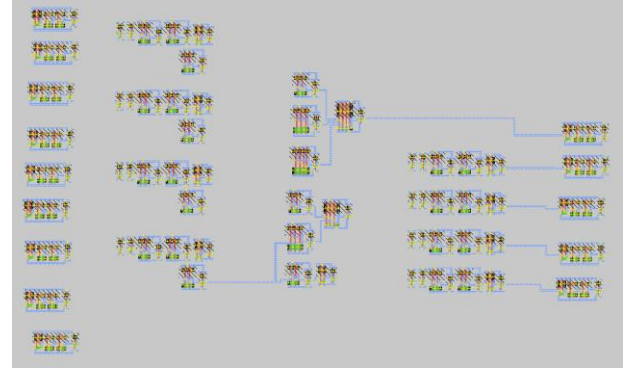


Fig. 34. Final circuit MAGIC layout

This is the complete floor plan of final circuit with Horizontal Pitch 167.13 μ m and Vertical Pitch 97.65 μ m with area 16320(μ m)².

IX. POST LAYOUT SIMULATIONS OF FINAL CIRCUIT

For A=1110 and B=1011 we get sum as 1001 and cout as 1 at the second positive edge of the clock. It matches with the pre-layout simulation.

 


Fig. 35. Final circuit (post layout)

X. DELAY OF CLA ADDER AND MAXIMUM CLOCK FREQUENCY

Worst case delay seen in pre-layout simulation is 0.8245ns.

For maximum clock frequency we find minimum clock time.

$$tclk_min = thold + tpd_max + tpcq_max$$

$$tclk_min = 0 + 0.82ns + 0.103ns = 0.823ns$$

Hence, $f_{max} = 1215.07$ MHz.

Maximum clock frequency at which our circuit operates correctly is 1215.07 MHz.

	Pre-layout	Post-layout
tclk_min	0.807ns	0.823ns
fclk_max	1239.16 MHz	1215.07 MHz

Table 2. tclk_min and fclk_max comparison

Post layout time is more than pre layout time.

XI. VERILOG SIMULATIONS AND WAVEFORMS

This 4-bit carry-lookahead adder (CLA) consists of three main components: D flip-flops, a carry-lookahead adder, and a top-level module integrating the two. The D flip-flops are used to store input and output values, ensuring that data is synchronized with the clock signal. Each input bit of the 4-bit numbers (A and B) and the carry-in (Cin) is stored in separate flip-flops before being passed to the adder. Similarly, the output bits of the adder, including the sum (S[3:0]) and carry-out (Cout), are passed through another set of flip-flops to stabilize the output and synchronize it with the clock.

The core arithmetic operation is performed by the carry-lookahead adder. It computes the propagate and generate signals for each bit and uses these to calculate the carry signals hierarchically. The carry-lookahead logic allows faster addition by directly computing carries rather than waiting for sequential propagation. The use of D flip-flops at both input and output ensures proper timing synchronization, making the circuit suitable for clocked or pipelined systems.

A. CLA adder



Fig. 36. Adder verilog simulation

 


Fig. 37. Adder gtk waveform

B. D flip flop

For verilog simulation we take D flip flop and not TSPC flip flop.

 


Fig. 38. D flip flop verilog simulation

 


Fig. 39. D flip flop gtk waveform

C. Circuit

 


Fig. 40. Circuit verilog simulation

 


Fig. 41. Circuit gtk waveform

XII. FPGA AND OSCILLOSCOPE WAVEFORM

We take inputs as A=1110 and B=1011 and on using FPGA and oscilloscope we get carry as 1, s3=1, s2=0, s1=0 and s0=1 which is our desired output. Hence our waveforms below are correct.

 


Fig. 42. Carry = 1

 


Fig. 43. s3 = 1 (yellow) and s2 = 0 (green)

 


Fig. 44. s1 = 0 (yellow) and s0 = 1 (green)

 


Fig. 45. Boolean board



Fig. 46. Setup of oscilloscope

ACKNOWLEDGMENT

I extend my sincere gratitude Prof. Abhishek Srivastava for entrusting me with this remarkable project, which offered an invaluable opportunity for learning. Furthermore, I appreciate the invaluable guidance provided by the TAs throughout the duration of this project.

REFERENCES

- [1] Digital logic and computer design by Morris mano.
- [2] Class Notes and Tutorial slides.

